

Lecture - 6

Verilog Modeling

Behavioral

How a system is working?

Structural

How a sys is constructed?

* Behavioral Modeling

* Example: 16:1 Multiplexer

```
module mux16to1 (in, sel, out);
```

```
    input [15:0] in;
```

```
    input [3:0] sel;
```


```
    output out;
```

```
    wire [3:0] t;
```

```
    assign out = in[sel]; // Equivalent to accessing
```

```
endmodule
```

// element of an array

 

Note: In above example, we have only specified the behavior of a 16:1 multiplexer.

* Write similar codes for the following:

1) 8:1 MUX, 4:1 MUX

2) 4:2 Encoder, 8:3 Encoder

3) 2:4 Decoder, 3:8 Decoder

★ If-Else statement

- if-else should be used only inside "always" block

Syntax:

1) if (condition)

begin

statements

end

2) if (condition)

begin

statements

end

else

begin

statements

end

3) if (condition)

begin

statements

end

else if (condition)

begin

statements

end

else

begin

statements

end

* ~~@~~ always @

* syntax:

always @ (sensitivity list)

begin

statements;

end

* Non-Blocking Assignment (\leftarrow)

always @ (a, b, c, d)

begin

b \leftarrow a;

c \leftarrow b;

d \leftarrow c;

} Concurrent execution

end

* Blocking Assignment (=)

always @ (a, b, c, d)

begin

b = a;

c = b;

d = c;


} Sequential execution

end

★ Structural Modeling

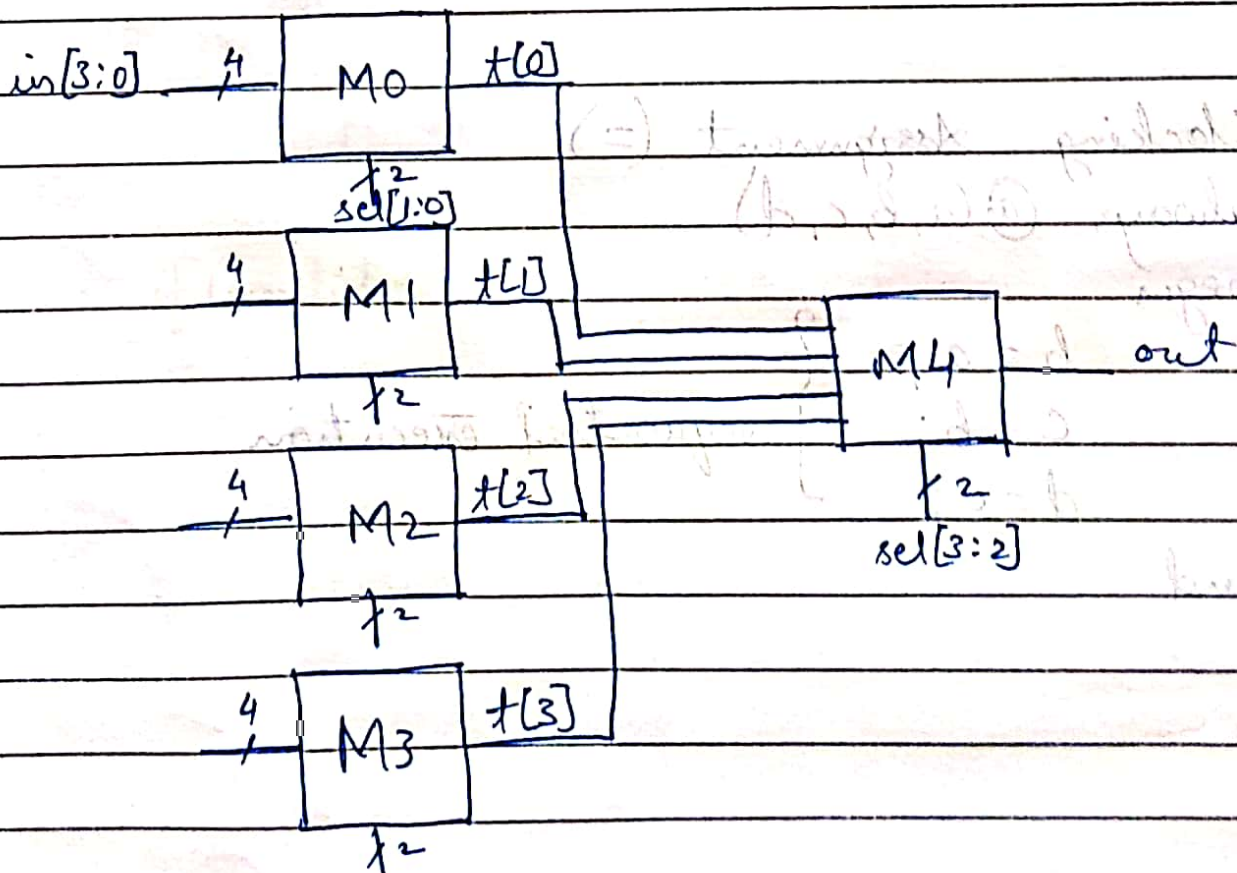*Example: 16:1 MUX using only 4:1 MUX

```
module mux16to1(in, sel, out);  
    input [15:0] in;  
    input [3:0] sel;  
    output out;  
    wire [3:0] t;  
    mux4to1 M0(in[3:0], sel[1:0], t[0]);  
    mux4to1 M1(in[7:4], sel[1:0], t[1]);  
    mux4to1 M2(in[11:8], sel[1:0], t[2]);  
    mux4to1 M3(in[15:12], sel[1:0], t[3]);  
    mux4to1 M4(t, sel[3:2], out);  
endmodule
```



* 4:1 MUX using behavioural style

```
module mux4to1 (in, sel, out);
```

```
    input [3:1] in;
```

```
    input [1:0] sel;
```

```
    output out;
```

```
    assign out = in[sel];
```

```
endmodule
```

* 2:1 MUX using structural modeling

```
module mux2to1 (in, sel, out)
```

```
    input [1:0] in;
```

```
    input sel;
```

```
    output out;
```

```
    wire t1, t2, t3;
```

```
    NOT g1(t1, sel)
```

```
    AND g2(t2, in[0], t1);
```

```
    AND g3(t3, in[1], sel);
```

```
    OR g4(out, t2, t3);
```

```
endmodule
```

