

Lecture - 8

★ Verilog Description Styles

Two different styles of description:

1) Dataflow

- continuous assignment

2) Behavioral

- procedural statements
 - blocking
 - non-blocking

★ Dataflow Style

- "assign" is used
- assign net-type-variable = net-type-variable;

assign net-type-variable = register-type-variable;

- The assignment is continuously active so it is used to model combinational circuits.
- A verilog code can contain any number of "assign" statements

```

module
    [signal declaration
    [assign statements
    [other statements (will be discussed later)
endmodule

```

Typical structure of a Verilog code

* Example:

```

module generate MUX (data, select, out);
    input [15:0] data;
    input [3:0] select;
    output out;
    assign out = data [select];
endmodule

```

Q] What will be the corresponding hardware synthesized?

- • Non-constant index in an expression on R.H.S. generates a MUX.
- If a constant index is present (Eg: assign out = data[2];) just a wire will be generated.


* Example:

```





module generate sel of MUX(a, b, f, sel);
    input [0:3] a, b;
    input sel;
    output [0:3] f;
    assign f = sel ? a : b;
endmodule

```

Conditional operator
generates a MUX

 


OR

    

Note: A conditional assignment always generates a 2:1 MUX

 • assign $f = (a == 0) ? (c + d) : (c - d);$




*Example:

```

module generate_decoder(out, in, select);
    input in;
    input [0:1] select;
    output [0:3] out;
    assign out[select] = in;
endmodule

```

 

Note:

- Non-constant index in an expression on LHS generates a decoder.
- Constant index in the expression on the LHS will simply generate a wire connection.

*Example:

```

module level-sensitive latch(D, Q, En);
    input D, En;
    output Q;
    assign Q = en ? D : Q;
endmodule

```

En	D	Q _n
0	X	Q _{n-1}
1	0	0
1	1	1

Note: A latch is generated if previous value of a variable is assigned to itself.