 


Lecture - 7

★ Example: A 16 bit ALU



```


module ALU(X,Y,Z,sign,zero,carry,parity,overflow);
    input [15:0] X,Y;
    output [15:0] Z;
    output sign,zero,carry,parity,overflow;
assign {C,Z} = X+Y;
    assign {carry,Z} = X+Y;
    assign sign = Z[15];
    assign zero = ~|Z;
    assign parity = ~^Z;
    assign overflow = (X[15] & Y[15] & ~Z[15]) |
                     (~X[15] & ~Y[15] & Z[15]);
endmodule

```


→ overflow occurs in 2 conditions

- 1) Addition of 2 -ve nos. is +ve no.
- 2) Addition of 2 +ve nos. is -ve no.

i.e.

 

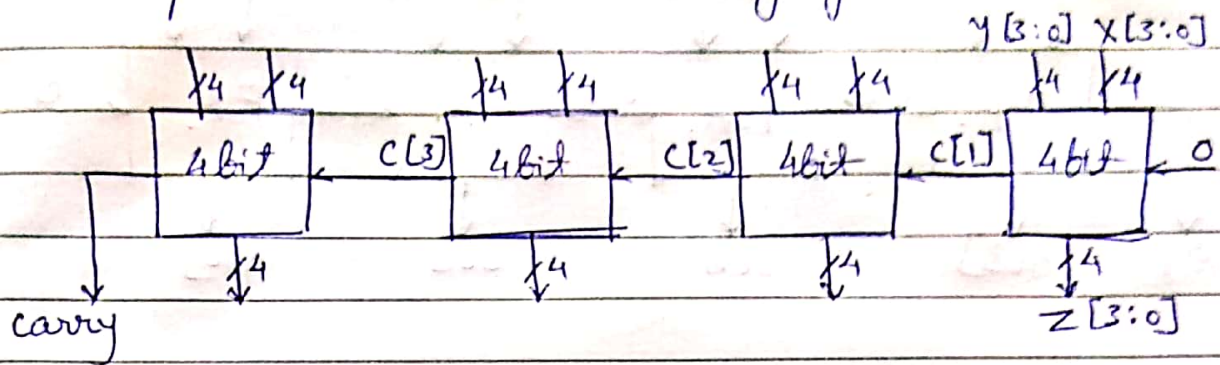★ Example: 16 bit adder using four 4 bit adders



```
module adder16(X,Y,Z,carry);
    input [15:0] X,Y;
    output [15:0] Z;
    output carry;
    wire c[3:1];
    adder4 A0(Z[3:0], c[1], X[3:0], Y[3:0], 1'b0);
    adder4 A1(Z[7:4], c[2], X[7:4], Y[7:4], c[1]);
    adder4 A2(Z[11:8], c[3], X[11:8], Y[11:8], c[2]);
    adder4 A3(Z[15:12], carry, X[15:12], Y[15:12], c[3]);
endmodule
```

★ Example: 4 bit adder using behavioral style

```
module adder4(S,cout,A,B,cin);
    input [3:0] A,B;
    output [3:0] S;
    input cin;
    output cout;
    assign {cout,S} = A+B+cin;
endmodule
```

★ Write a verilog code for 4 bit binary adder using structural style.

