

★ Complex Programmable Logic Devices (CPLD)
 - reference → NPTEL, Digital System Design, IISC,

* PLD → SPLD → simple
 ↓
 CPLD

* Idea → Memory as programmable logic in 80's

→ PROM → Programmable m/m

* Eg: XOR gate using PROM

~~X 7~~

	00	0
X — A ₁	01	1
Y — A ₀	10	1
	11	0

OR

	1B each
11	0
10	1
01	1
00	0

↑ Address ↑ content at the address


m/m in read mode

Addⁿ lines → i/p

Data line → o/p

Truth table → content.

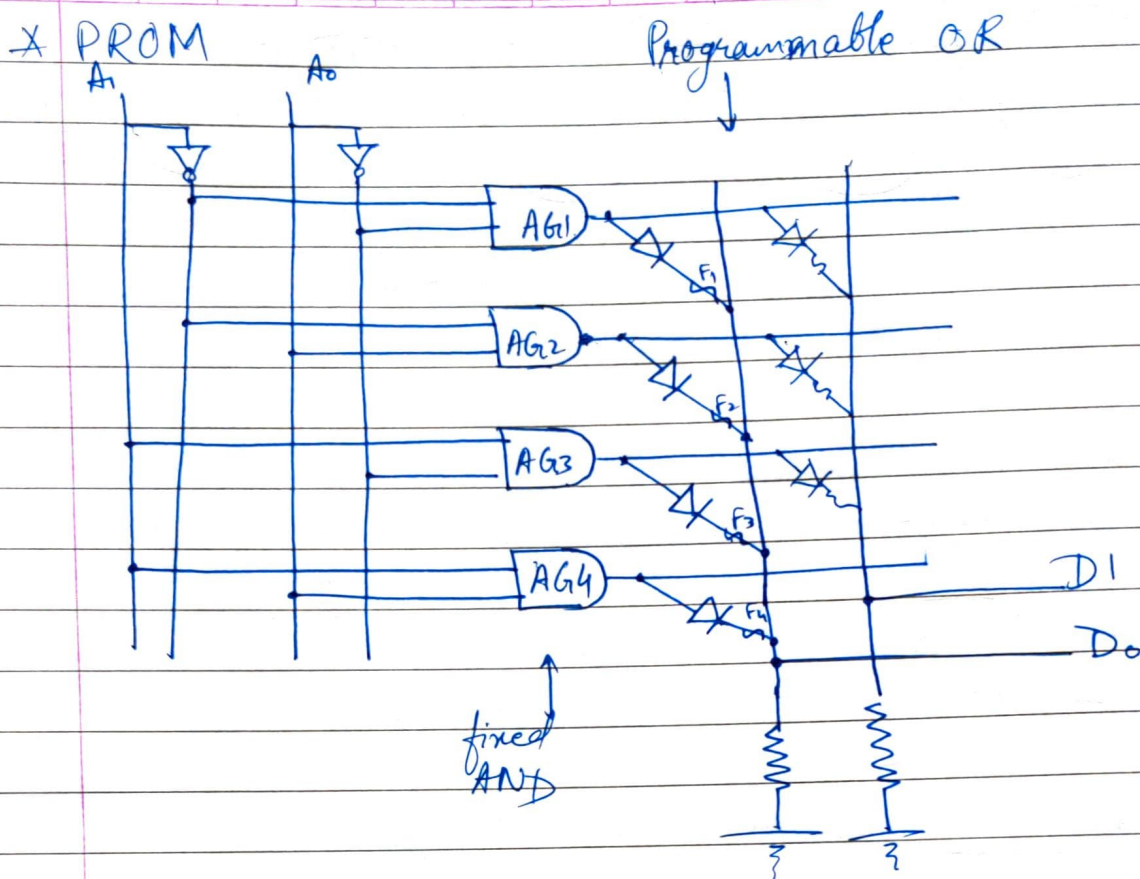NOTE: # M/m should be non-volatile so that the T.T. or the contents are not lost.



F: fuse

- blow fuses $F1$ & $F4$ (for XOR gate example). (How to blow is not necessary).
- blowing fuse = programming 0.
- when $A1A0 = 00$, $AG1$'s $o/p = 1$ but $F1$ is blown so 1 does not get connected to $D0$ i.e. $D0$ is pulled down to 0 (gnd).
- when 10, $D0$ becomes 1.
- If ~~if~~ no. of ~~inputs~~ $= n$ then no. of AND gates $= 2^n$

Q] What is the use of diode?

→ $A1A0 = 10$, o/p of $AG2 = 1$ & $AG3 = 0$, In absence of diode, $AG2 = AG3$ i.e. we are shorting 2 lines have $+V_{cc}$ & GND level!

Q] How to blow the fuse?

→ Apply $-ve$ voltage to $D0$, provide proper $A1A0$. So the current exceed fuse rating current then the fuse is blown.


No. of AND gates required = $2^{(\text{no. of i/p's})}$

Q] Can we ~~req~~ reduce the no. of AND gates?

→ Yes, but the AND gates should be programmable
& Minterms → Product terms

↳ This is the the beginning of PLA.

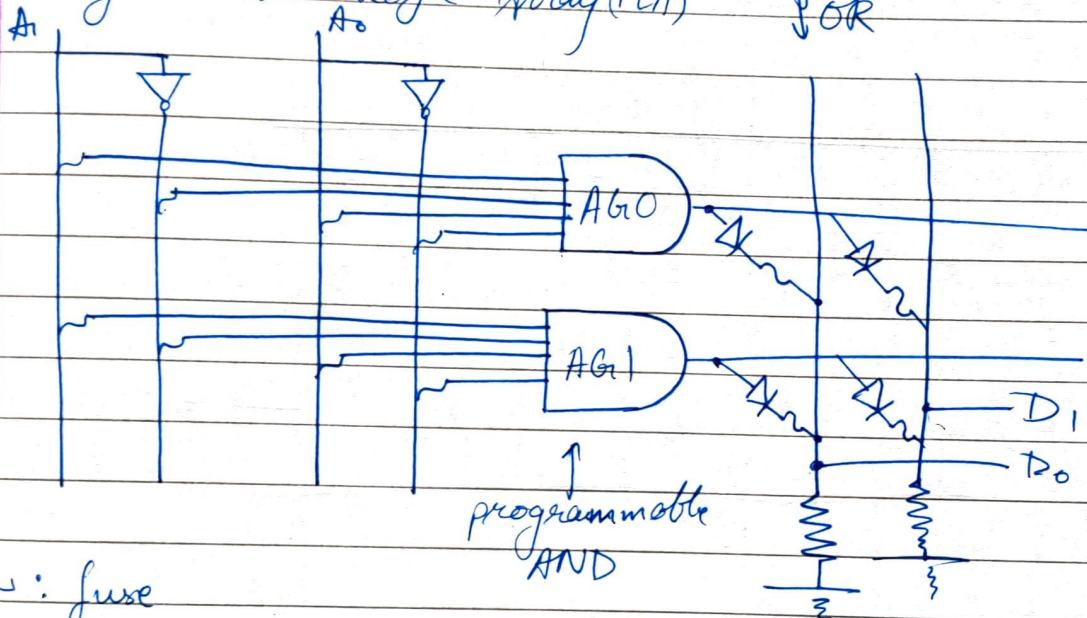
★ Programmable Logic Array (PLA) programmable AND OR



~: fuse

AG0 & AG1 will give $op=1$ for $A_1A_0 = 01$ or 10 i.e. XOR

★ Programmable Array Logic (PAL)

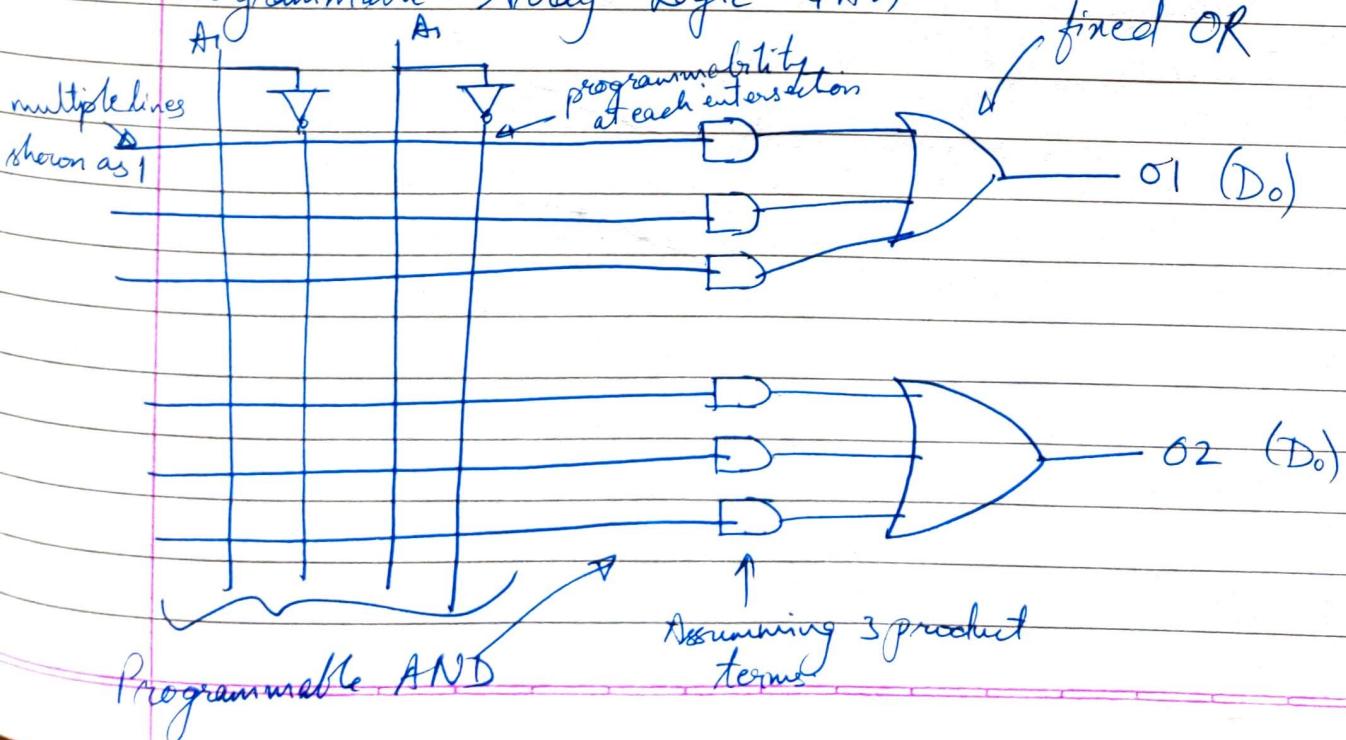

★ PAL is the real architecture of PLD.

- ★ PAL:
- 1) programmable AND
 - 2) fixed OR
 - 3) dedicated product terms for outputs.

~~PROM: fixed AND~~

	AND	OR	
PROM	fixed (F)	programmable (P)	
PLA	P	P	
PAL	P	F	→ = CPLD

★ Check PAL16L8 on net for idea of PAL

→ Texas Instruments

→ This is a practical example of SPLD.

- * Limitation of CPLD:
- ① Large no. of switches are required
 - ② Complex design
 - ③ Many product terms are rarely used but still a AND gate is allocated

* CPLD VS FPGA

Feature	PLD	FPGA
1) Logic	AND-OR	MUX/LUT/Gates
2) Register to logic ratio	small (low m/m)	large
3) Timing	simple	complex
4) Architecture variation	small	large
5) Programming technology	flash	anti-fuse, SRAM
6) Capacity	10K	few million logic cells + few MB RAM.

* FPGA

ASIC → Built from scratch, large cost & time, high design cost (NRE: Non recurring expenditure).

MPGA (Mask Programmable Gate Array)

- Array of transistors
- Interconnections are made ~~in~~ during fabrication & cannot be altered on "FIELD".

FPGA → Programmable ^{interconnections} on field.
→ Array of logic resources

* Logic Resources: LUT (similar to CPLD concept)
Multiplexers
Registers

* Programmable Interconnections: SRAM

Flash transistor

Anti-Fuse (opp. of a fuse) (make connection by applying voltage)

* Special Resources: PLL/DLL, RAMs, FIFOs
↳ Delay Locked Loop

* Memory Controllers, Network Interfaces, Processors (in complex FPGAs)

★ Commercial FPGA (main manufacturers)

- Xilinx

- spartan-3, -4, -6 : Low cost FPGA

- Virtex-4, -5, -6 : complex FPGA (previous gen.)

- Artix-7, Kintex-7, Virtex-7, Zynq : current generation

- Altera


- Cyclone, -10, -10L, -10B, -10C : Low cost

- Arria 10, 10V :

- Stratix 10, 10GX, 10K, 10M :

} Complex versions

* Structure of a FPGA

 

- * Pins: VCC, GND, I/O
- * Logic block: Small logic & flipflops
- * Lot of interconnections b/w logic blocks.
- * Interconnections delay may be $>$ logic computation delay.
but large interconnections provide flexibility.
- * Interconnections: Switch blocks

