

Lecture - 4

★ Recap: Register Data Types

- reg
- integer
- real
- time

- Vectors
- Multidimensional Arrays & Memories
- Constant values
- Parameters (Equivalent to #define)

★ Predefined Gates in Verilog

- Verilog supports 4 logic values: 0, 1, X, Z

Gates: AND, OR, NOT, XOR

★ Laboratory Assignment (To be submitted via mail)

* Write verilog codes to verify o/p of the following:

1 & x	1 x	1 ^ z
0 & x	1 z	0 ^ x
1 & z	0 x	1 ^ x
0 & z	0 z	0 ^ z

★ List of Primitive Gates

and G(out, in1, in2);

nand G(out, in1, in2);

or G(out, in1, in2);

nor G(out, in1, in2);


xor G(out, in1, in2);

xnor G(out, in1, in2);

not G(out, in);

buf G(out, in);

bufif1 G(out, in, ctrl);

 

```
if ctrl = 1
```

```
out = in
```

```
else
```


```
out = z
```

```
end
```



```
bufif0 G(out, in, ctrl);
notif0 G(out, in, ctrl);
notif1 G(out, in, ctrl);
```

* Example: 5 i/p AND gate:

 

```
AND G(out, a, b, c, d, e);
```

* Restrictions while instantiating primitive gates:

- output port must be connected to a net (Eg: a wire) (output signal is a wire by default)
- input port may be connected to NET or REGISTER type variable.

• primitive gates (except not/buf) can have a single o/p but any no. of i/p's.

- optional delay can be added as follows:

```
and #5 G1(f, a, b);
```

↳ this delay is used only for simulation
(#5 means time specified on time scale.)

* Example:

timescale 10ns/1ns

```
module exclusive_or (f, a, b);
```

```
input a, b;
```

```
output f;
```


```
wire t1, t2, t3;
```

```
nand #5 m1(t1, a, b);
```

```
and #5 m2(t2, a, t1);
```

```
and #5 m3(t3, t1, b);
```


```
endmodule nor #5 m4(f, t2, t3);
```

 

- 'timescale 10ns / 1ns
 basic unit of time so #1 = 10ns
 & #5 = 50ns
 precision of simulation (it is the precision to which delays are rounded)

- valid values for specifying time unit & time precision are 1, 10 and 100.
- valid units: s, ms, μ s, ns, ps, fs

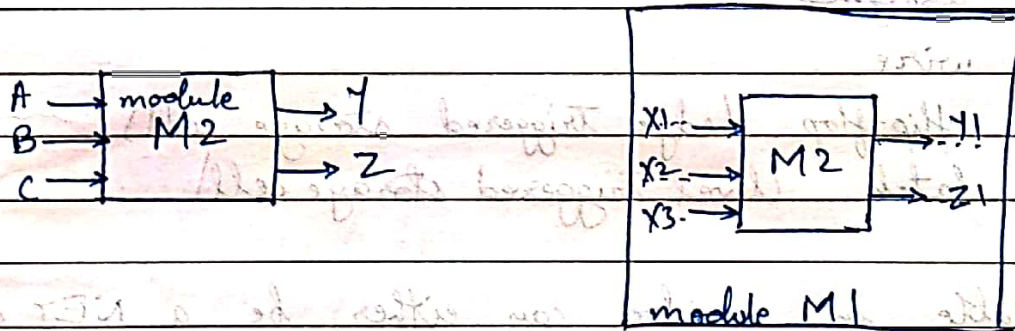★ Specifying Connectivity during Instantiation



- instantiation of one module inside another.
- Two ways to specify the connections:
 - a) Positional Association

The parameters of M2 are listed in same order as in the original module description

Eg:

```
module M2(A,B,C,Y,Z)
```

```
module M1(
```

```
    M2 DUT(X1,X2,X3,Y1,Z1);
```

```
endmodule
```

DUT: Device Under Test

b) Explicit Association

Parameters can be in arbitrary order. Here, chance of error is also less.

Eg:

```
module M1 (
    :
    M2 DUT(M1(Y), A1(A), C1(C), Z1(Z), B1(B));
endmodule
```

* Hardware Modeling Issues

* In terms of h/w realization, the computed value can be assigned to:

- a wire
- a flip-flop (edge triggered storage cell)
- a latch (level triggered storage cell)

* A variable in verilog can either be a NET or a REGISTER.

- NET always maps to a wire.
- REGISTER maps either to a wire or a storage cell.

★ Example:

```
module logic_ckt(a,b,c, f1, f2)
```

```
input a,b,c;
```

```
output f1,f2;
```

```
reg f1,f2;
```

```
always @ (a or b or c)
```


```
begin
```

```
    f1 = ~ (a & b);
```


```
    f2 = f1 ^ c;
```

```
end
```

```
endmodule
```

 

 // Execute this block if
// there is event on a, or b, or c.



★ Example:

```
f2 = f1 ^ f2;
```

```
f1 = ~ (A & B);
```

