

## Lecture - 10

### \* Procedural Assignment (contd.)

- \* Recap:
- while loop
  - for loop
  - repeat loop
  - # time-value
  - @ (event-expression)
  - Laboratory tasks

\* Example: 2:1 MUX using procedural style

```
module mux21 (in1, in0, s, f);  
    input in1, in0, s;  
    output reg f;  
    always @ (in1 or in0 or s)  
        if (s) // if (s=1)  
            f = in1;  
        else  
            f = in0;  
endmodule
```

• A 2:1 MUX will be synthesized.

• always @ (in1 or in0 or ~~in3~~<sup>s</sup>);  
    // (equal)

always @ (in1, in0, s)  
    // (equal)

always @ (\*) // always block gets executed when  
                  // any of the "input" type variable  
                  // changes

~~Example~~ Example: A D type negative edge triggered flip-flop

```
module dff_negedge (D, clock, Q, Qbar);  
    input D, clock;  
    output reg Q, Qbar;  
    always @negedge clock  
    begin  
        Q = D;  
        Qbar = ~D;  
    end  
endmodule
```


\* Example: A 4 bit counter with asynchronous reset

```
module counter (clk, rst, count);  
    input clk, rst;  
    output reg [3:0] count;  
    always @ (posedge clk or posedge rst)  
    begin  
        if (rst)  
            count <= 0;  
        else  
            count <= count + 1;  
        end  
    end  
endmodule
```



\* Example: Determine the hardware generated / synthesized by the following codes

 
```
① module xyz (input a, b, c, output reg f);  
    always @(*)  
        if (a == 1)  
            f = b & c;  
endmodule
```



Note: New compilers of verilog support the following format

```
module xyz (input a, b, c, output reg f);
```
 
```
② module xyz1 (input a, b, c, output reg f);  
    always @(*)  
    begin  
        f = c;  
        if (a == 1)  
            f = b & c;  
    end  
endmodule
```



H.W. Write a verilog code for an 8 bit priority encoder.